



Study of Chaos and Dynamics of DC-DC Converters

BY

SAI RAKSHIT VINNAKOTA

ANUROOP KAKKIRALA


VIVEK PRAYAKARAO

What are DC-DC Converters??

- ▶ A **DC-to-DC converter** is an electronic circuit which converts a source of direct current (DC) from one voltage level to another.

Types of DC-DC Convertors:

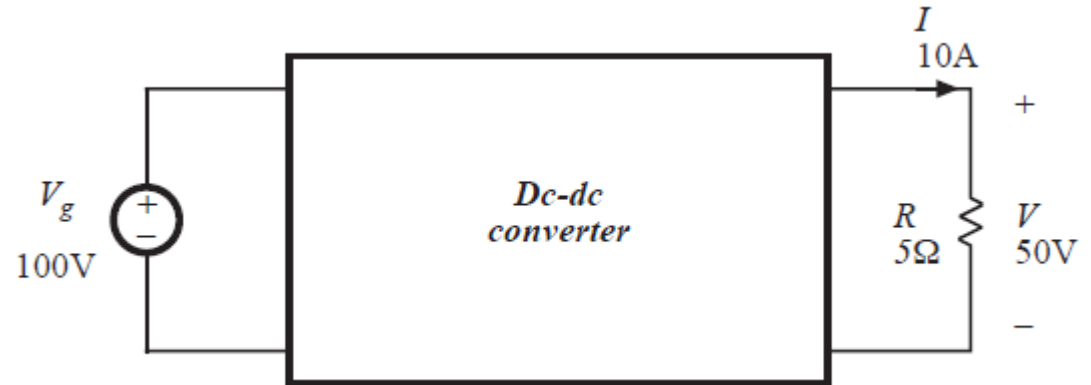- ▶ **Linear (Dissipative)**
- ▶ **Switched-mode conversion**
- ▶ **Magnetic**




Input source: 100V

Output load: 50V, 10A, 500W

How can this converter be realized?


Linear or Dissipative realization

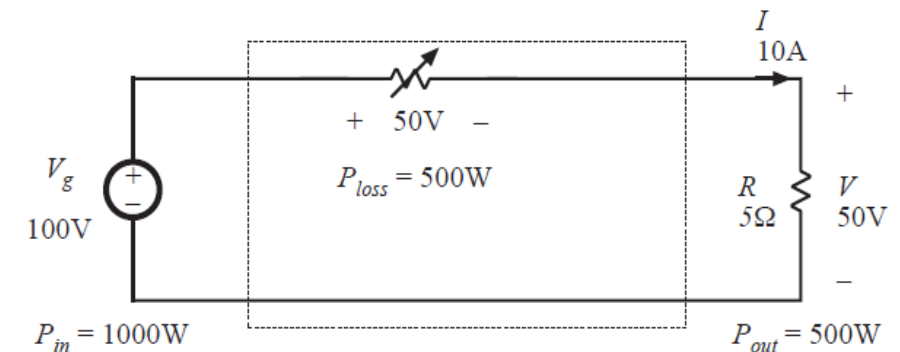- ▶ Linear regulators can only output at lower voltages from the input.
- ▶ They are very inefficient when the voltage drop is large and the current is high
- ▶ They dissipate heat equal to the product of the output current and the voltage drop.
- ▶ The inefficiency wastes power and requires higher-rated and consequently more expensive and larger components.



Switched-mode conversion

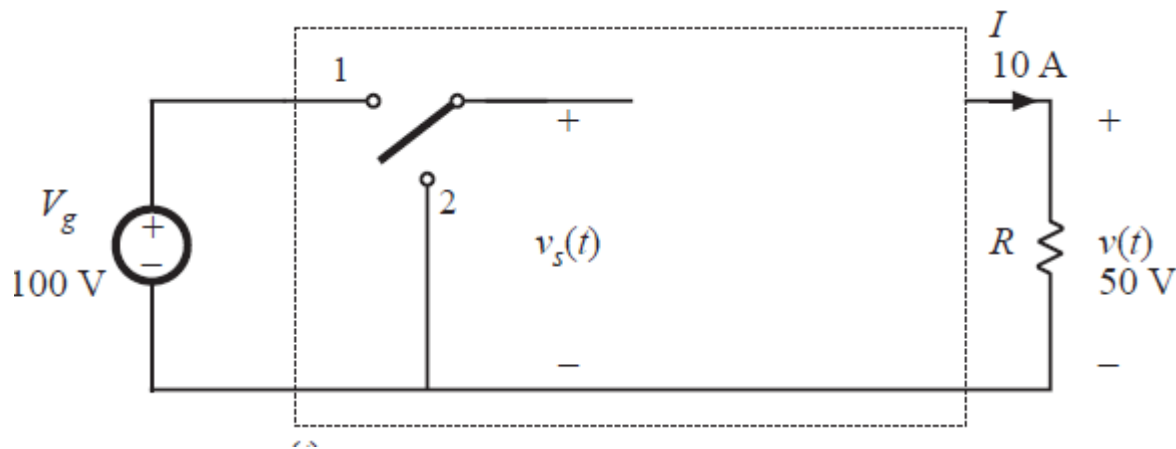- ▶ Electronic switch-mode DC to DC converters convert one DC voltage level to another, by storing the input energy temporarily and then releasing that energy to the output at a different voltage.
- ▶ This conversion method is more power efficient and is beneficial to increase the running time of battery operated devices.
- ▶ Drawbacks of switching converters include complexity, electronic noise.




Non Linearity !!

Why is it important to study the dynamics??

- ▶ The semiconductor switching devices have intrinsically nonlinear DC characteristics: BJTs, MOSFETs, IGBTs, thyristors, diodes.
- ▶ They also have nonlinear capacitances, and most suffer from minority carrier charge storage.
- ▶ The control circuits usually involve nonlinear components: comparators, pulse-width modulators (PWMs), multipliers etc.

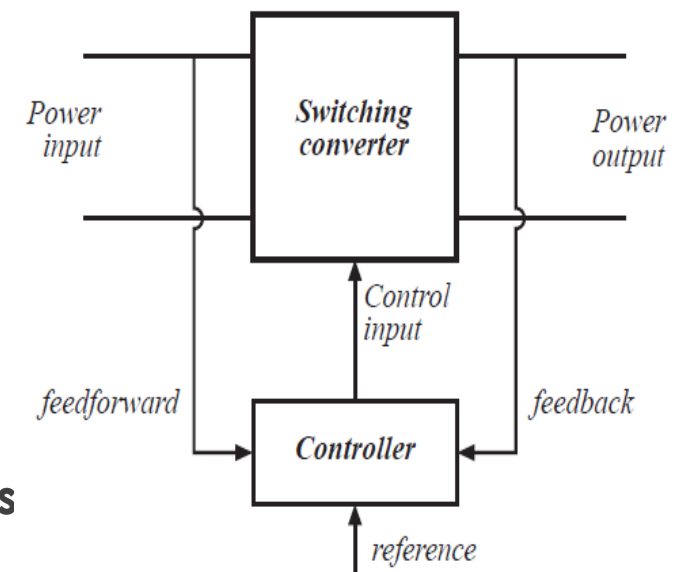So, study of dynamics and chaos in such circuits help in the design, analysis and control of power converters.



Types of DC-DC Converters

▶ Buck Converter

A **buck converter** (step-down convertor) is a DC -to- DC power converter with an output voltage less than its input voltage.



▶ Boost Converter

A **boost converter (step-up converter)** is a DC-to-DC power converter with an output voltage greater than its input voltage.

▶ Buck-Boost Chopper

A **buck-boost converter** is a DC-to-DC converter that has an output voltage magnitude that is either greater than or less than the input voltage magnitude.

Buck Converter

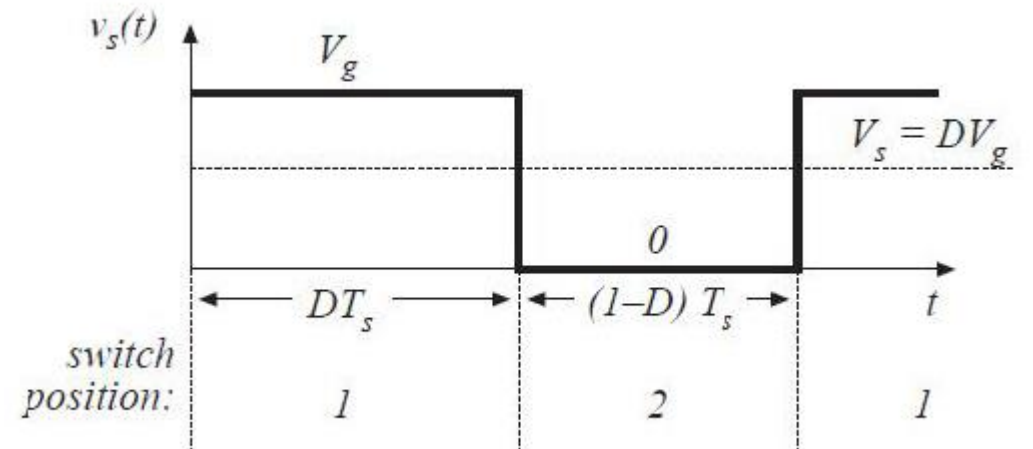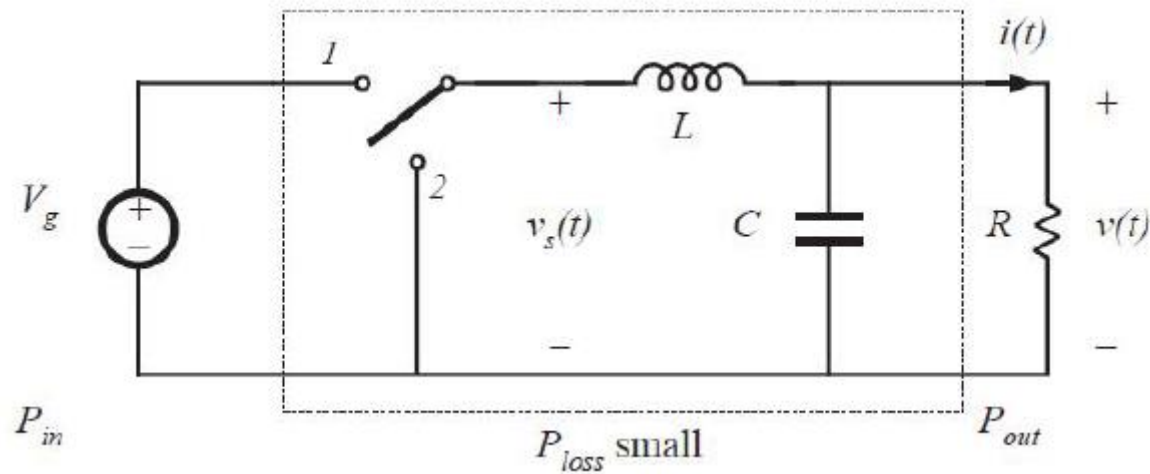

The average value of $v_s(t)$, which would then be equal to DV_g .
Therefore,

$$V_s = D V_g$$

Principle of Operation of a Buck Converter


- ▶ DC-DC Buck Converter exhibits a wide range of bifurcation and chaos phenomena even for small changes in the parameter values of the device.
- ▶ The differential equations governing the circuit are

$$\frac{dv}{dt} = \frac{-1}{C}i(t) - \frac{1}{RC}v(t)$$
$$\frac{di}{dt} = -\frac{1}{L}v(t) + \frac{E}{L}\delta(t)$$

$$V_c(t) = a(V(t) - V_{ref})$$

$$V_r(t) = V_L + (V_u - V_L)\frac{t \bmod T}{T}$$



Simulation of the Circuit

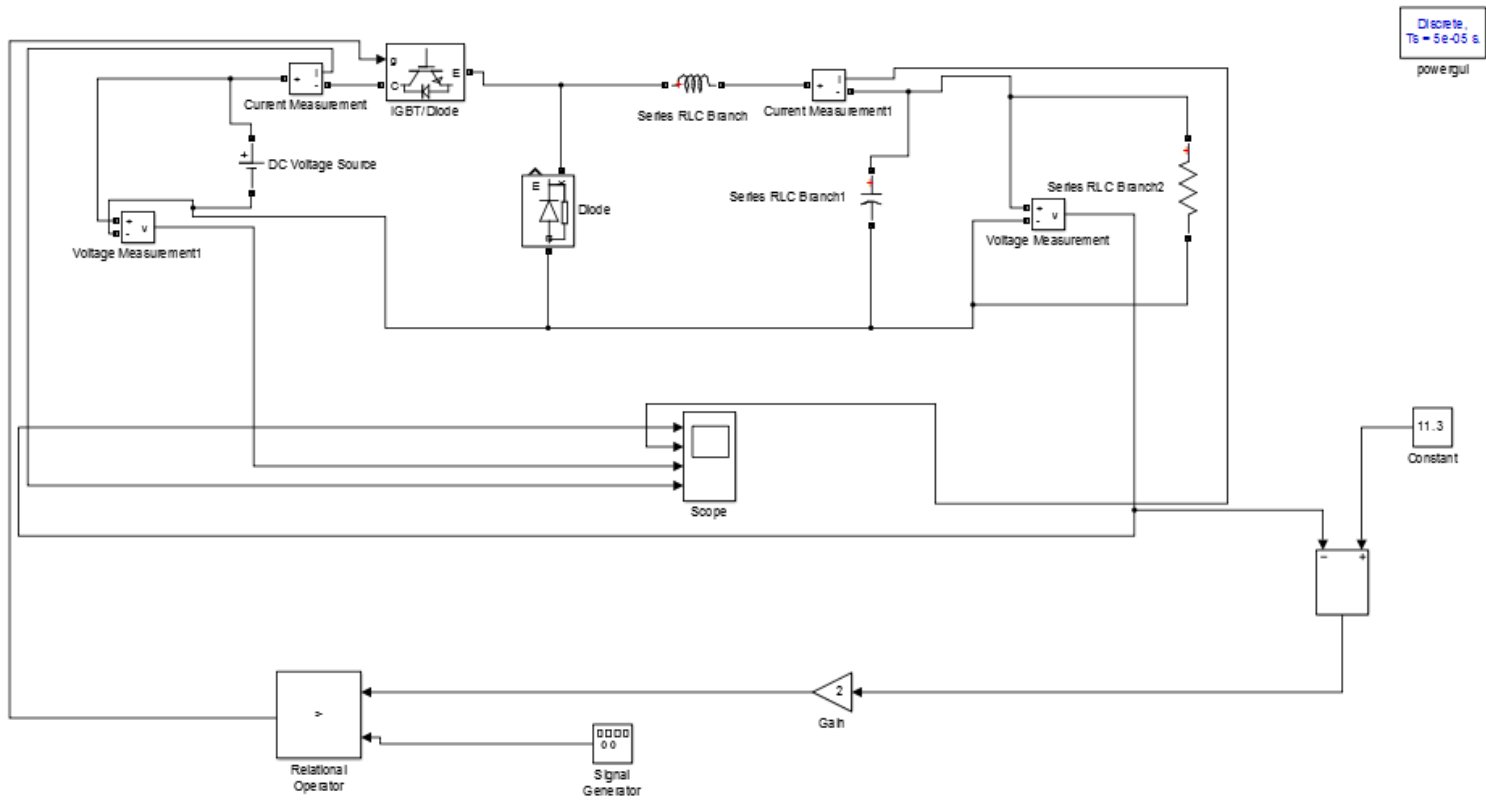

The parameters chosen are $V_{in} = 15V - 40V$, $V_{ref} = 11.3V$,
 $L = 10 \text{ mH}$, $C = 25 \mu\text{F}$, $R = 15 \Omega$,
 $\alpha = 2$, $V_L = 2V$, $V_U = 5V$, $T = 400 \mu\text{s}$;



Simulation Results

Period 1 at $V_i = 19.5\text{ V}$

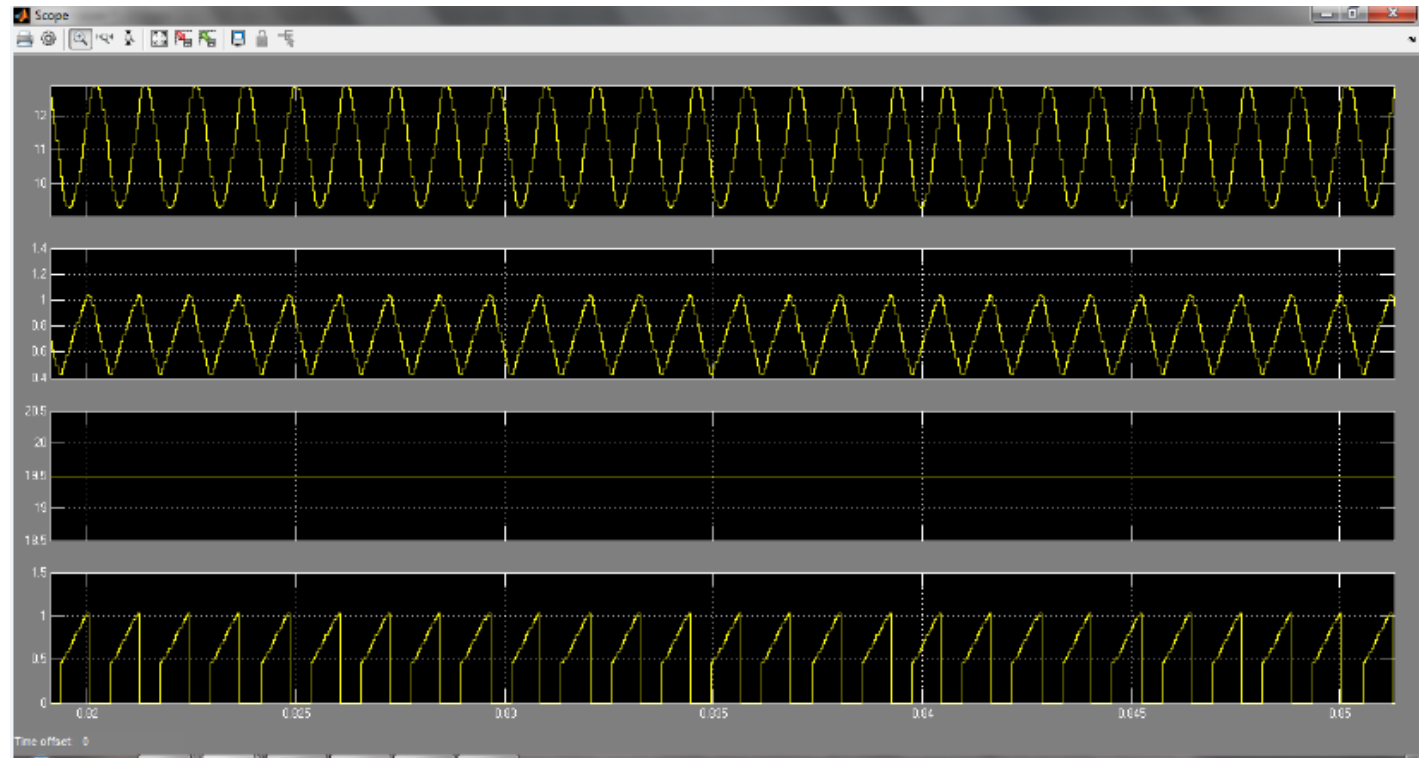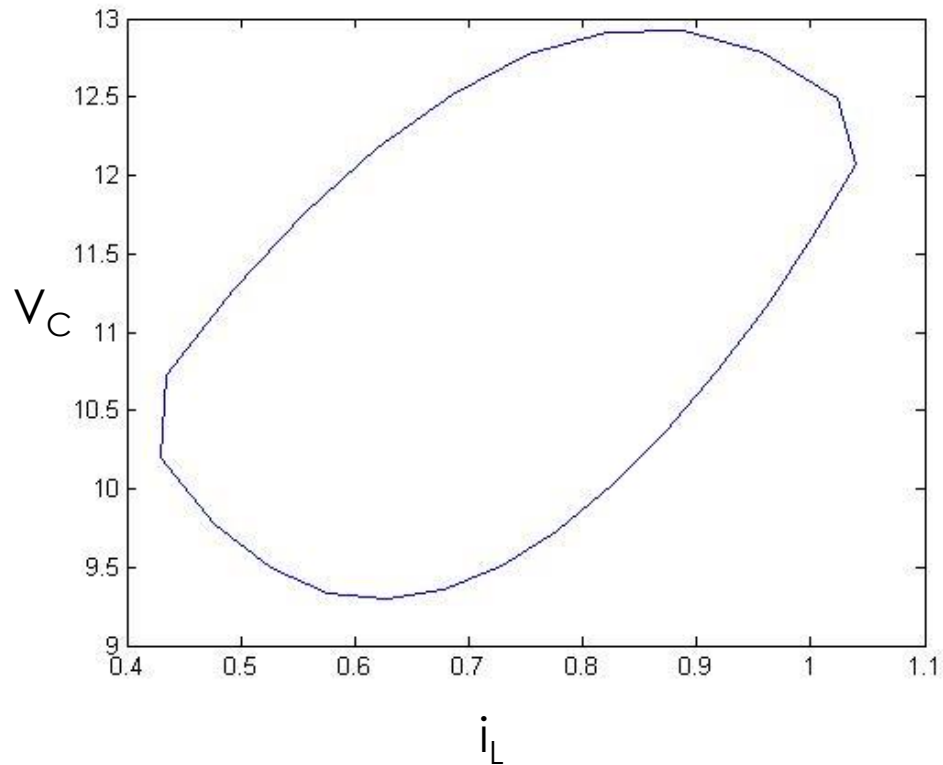



Simulation Results cont...

Period 2 at $V_i = 20\text{ V}$

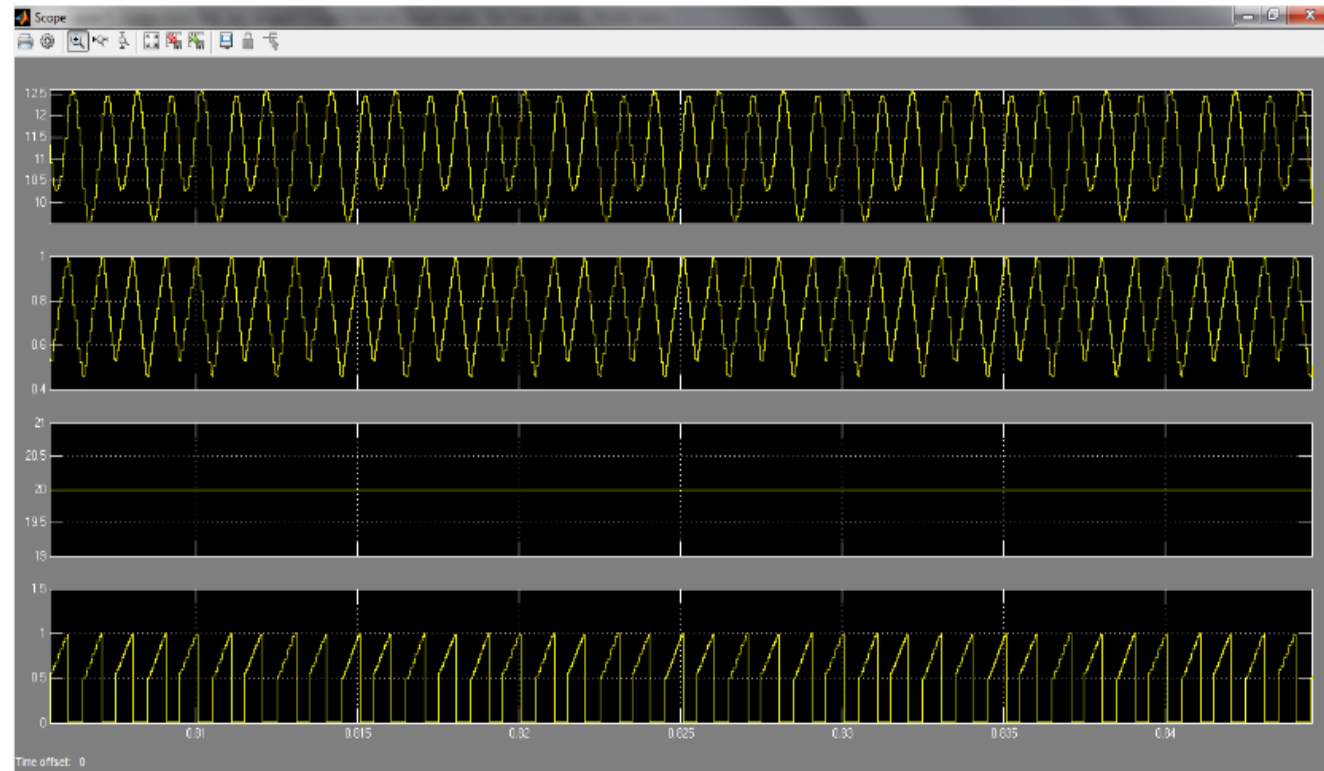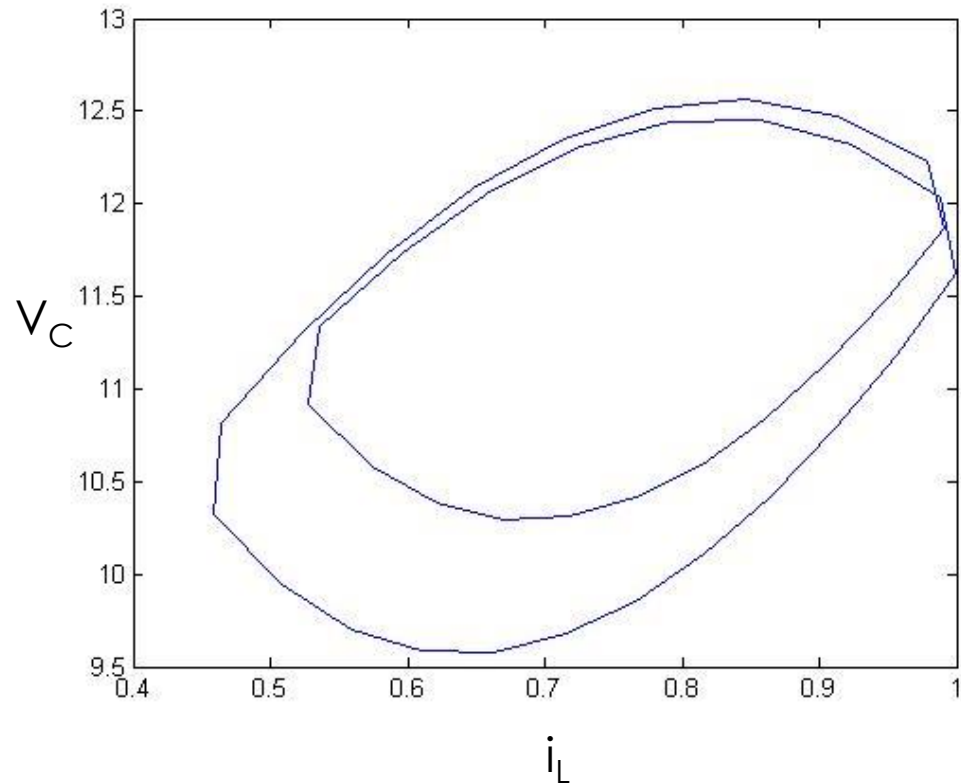



Simulation Results cont...

Period 3 at $V_i = 30\text{ V}$

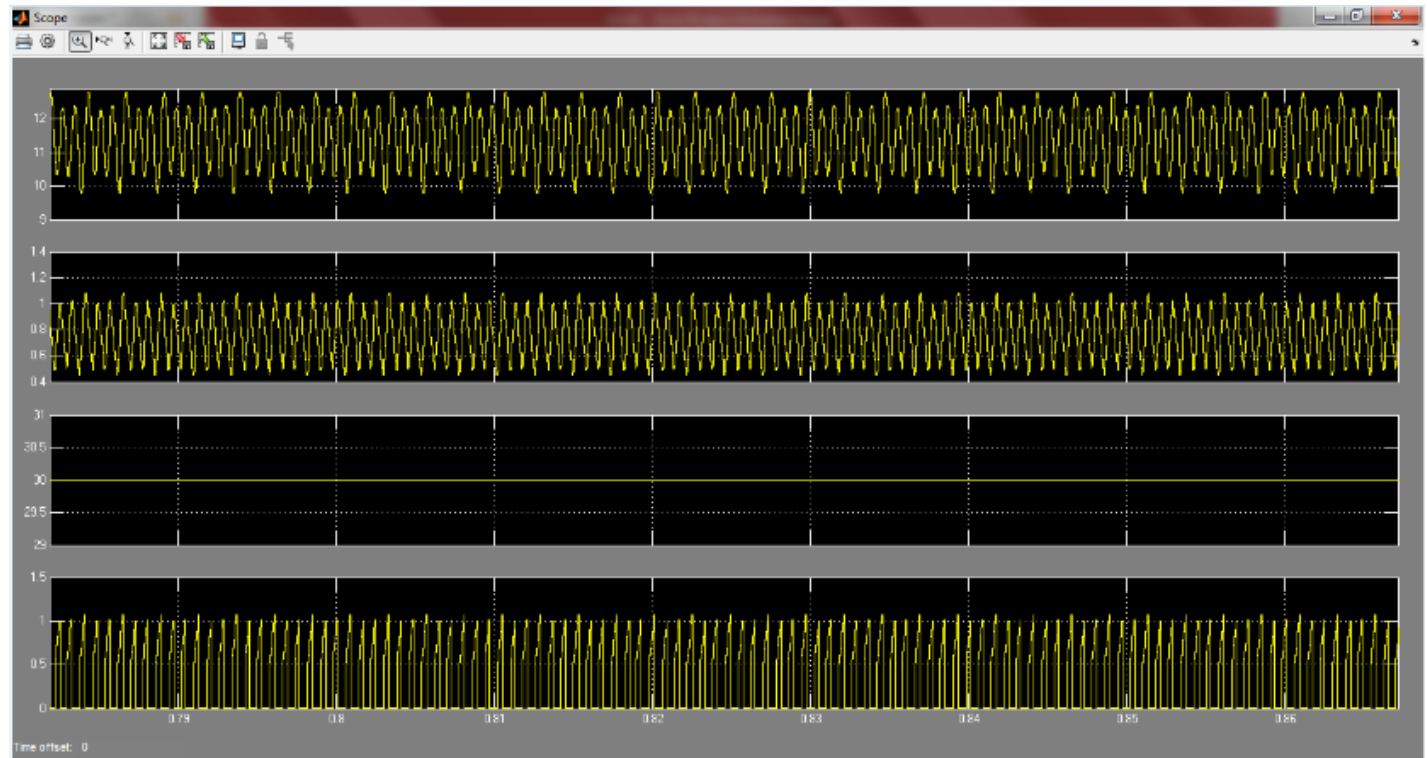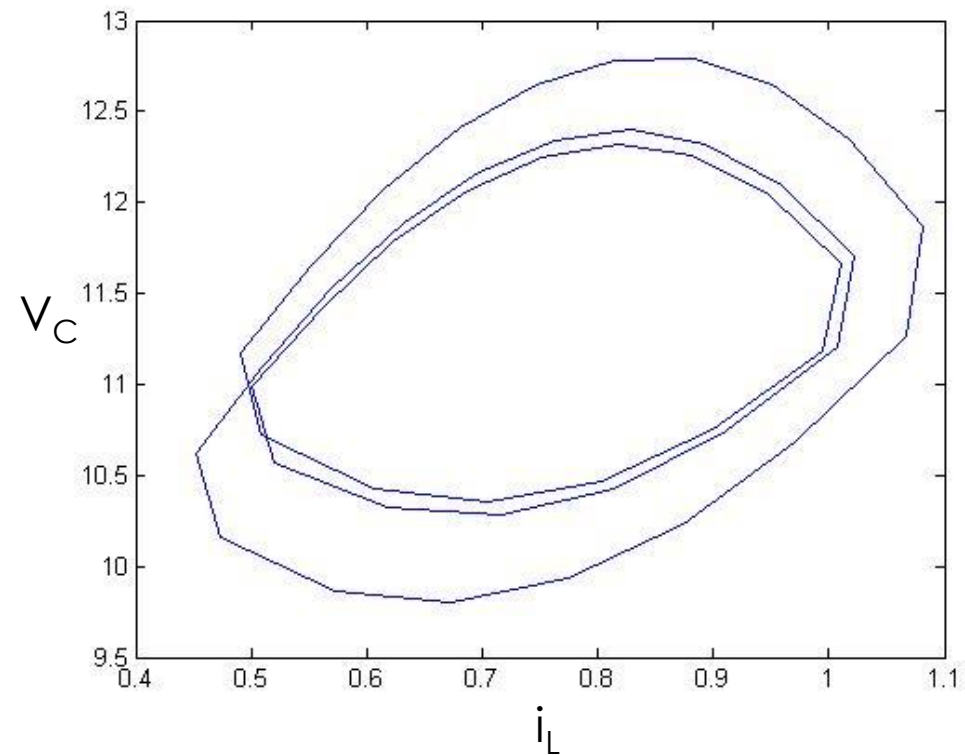


Simulation Results cont...

Chaos at $V_i = 33.5$ V

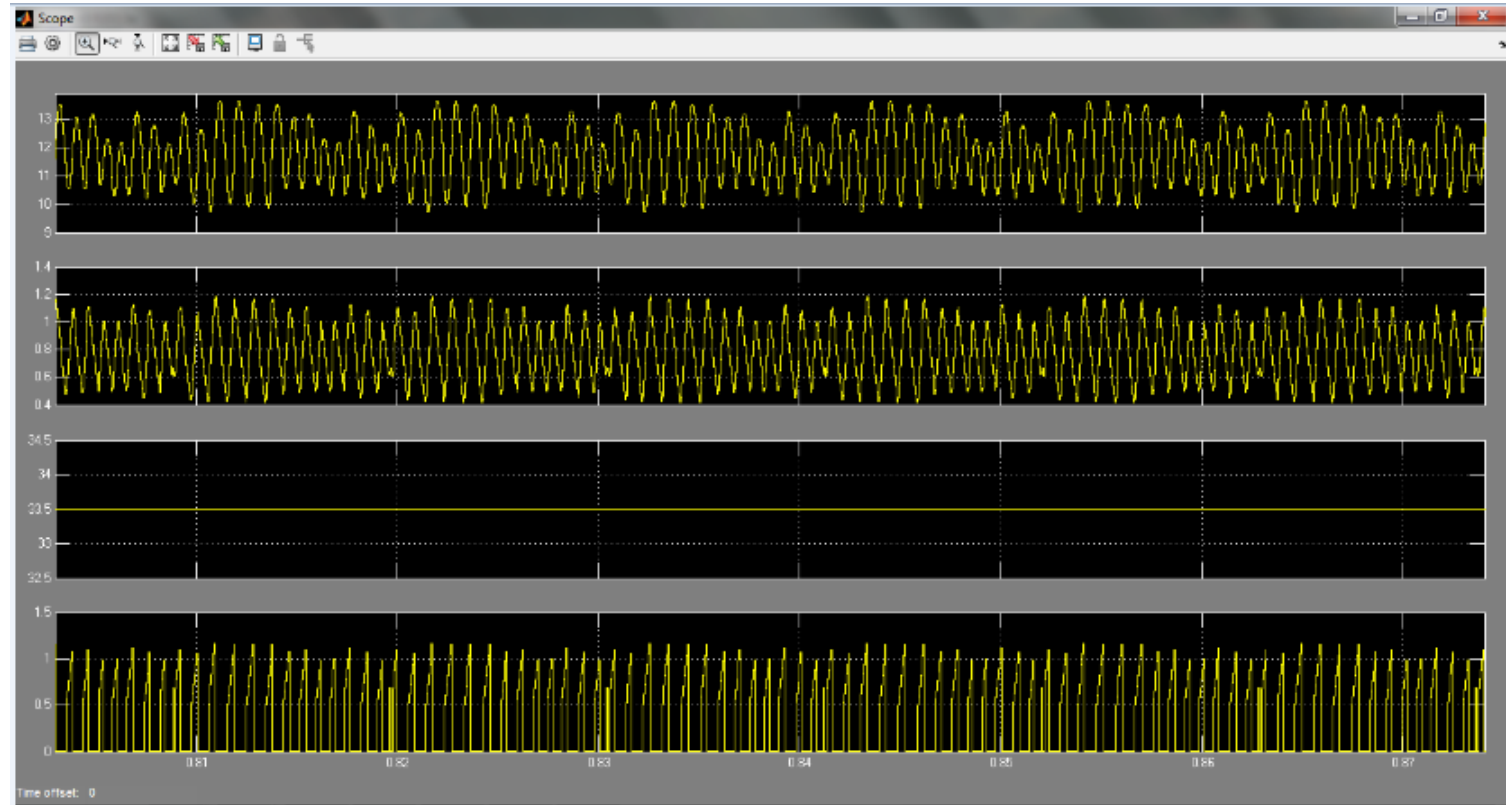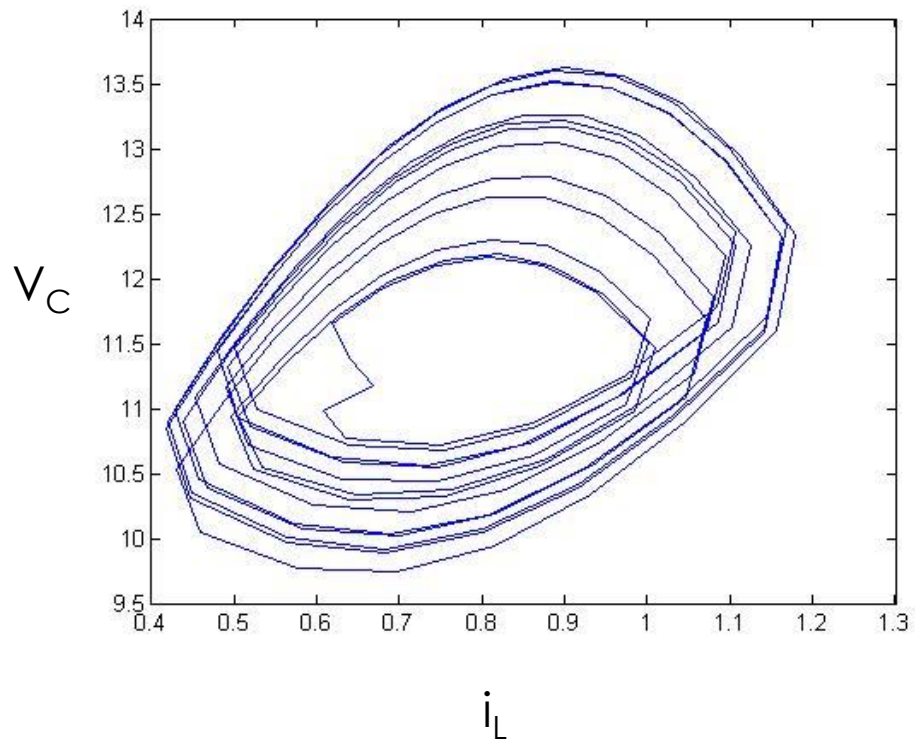


Bifurcation Diagram

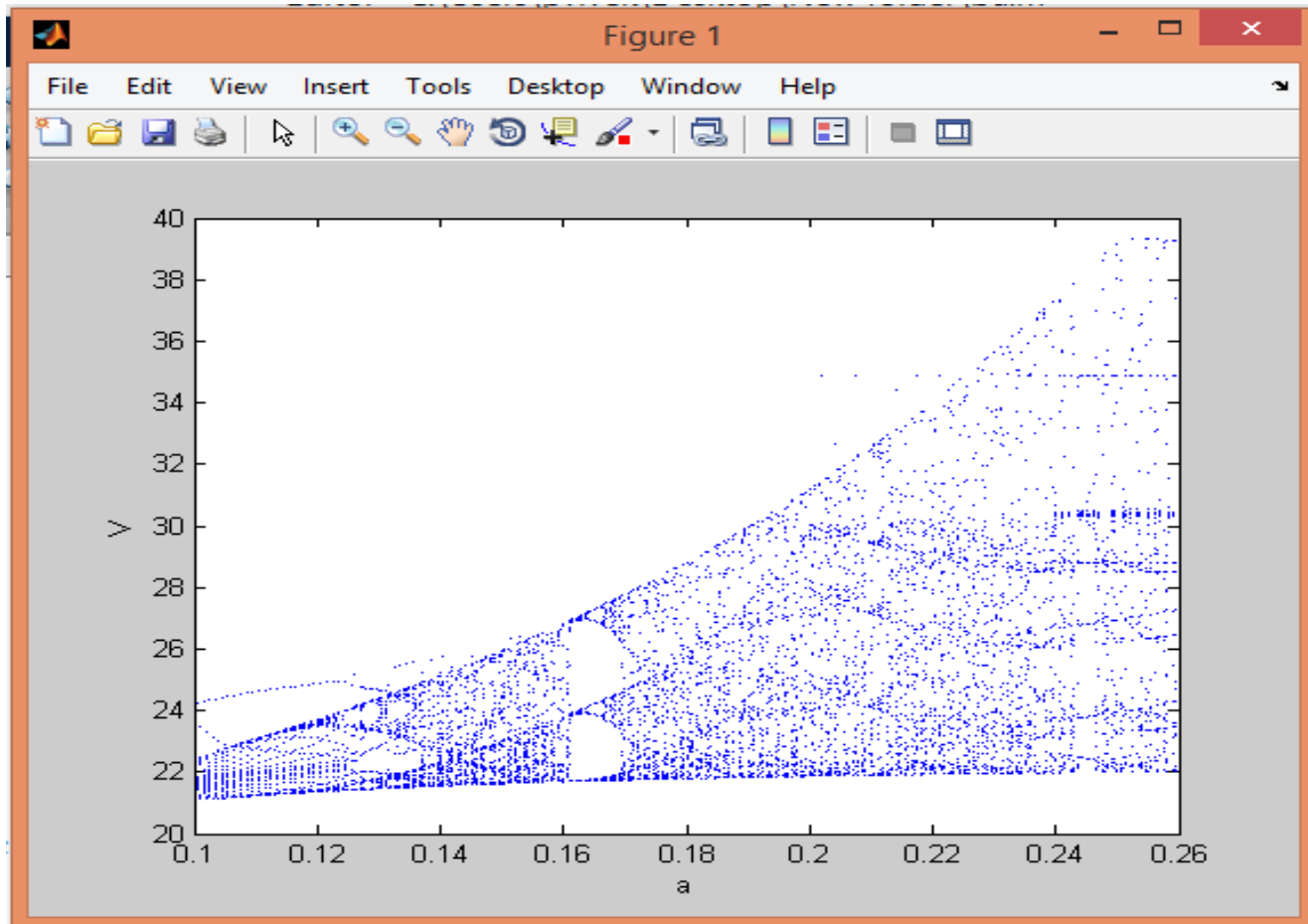

Gain 'a' was chosen as the bifurcation parameter. This diagram clearly shows that the period-doubling route to chaos is initiated as a reaches 0.22.

Boost Converter

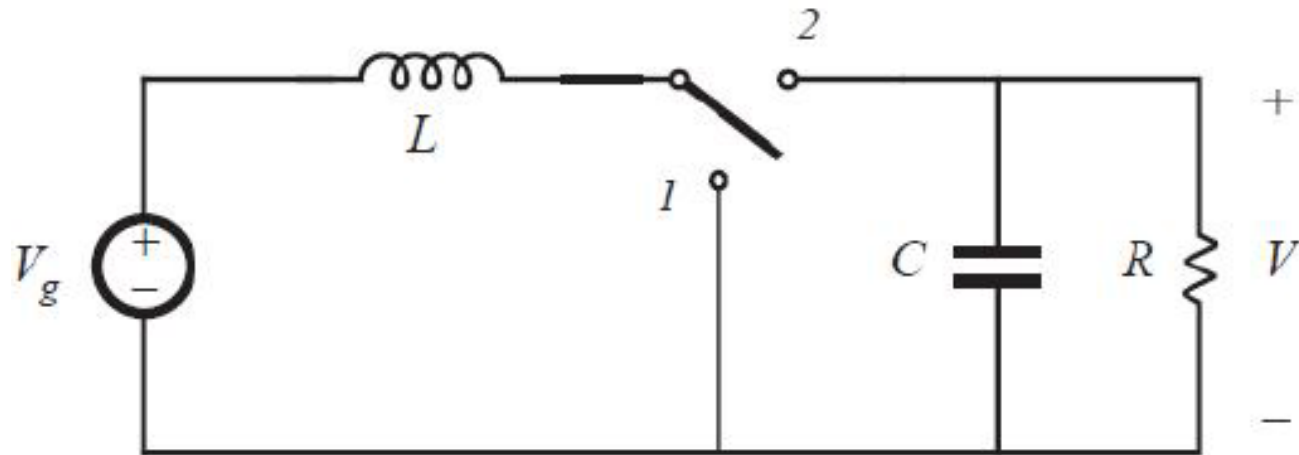

- The input-output relation for this boost circuit would be:

$$V_o = V_g / (1 - D)$$


Principle of Operation of a Boost Converter

- ▶ DC-DC Boost Converter exhibits a wide range of bifurcation and chaos phenomena even for small changes in the parameter values of the device.
- ▶ The differential equations governing the circuit are

$$\frac{d\hat{u}_C}{dt} = \frac{1}{RC} \left(\frac{kV_a^2}{V_m} - 1 \right) \hat{u}_C + \frac{V_m}{V_o C} \hat{i}_L$$

$$\frac{d\hat{i}_L}{dt} = -\frac{1}{L} \left(kV_o + \frac{V_m}{V_o} \right) \hat{u}_C$$



Simulation of the Circuit

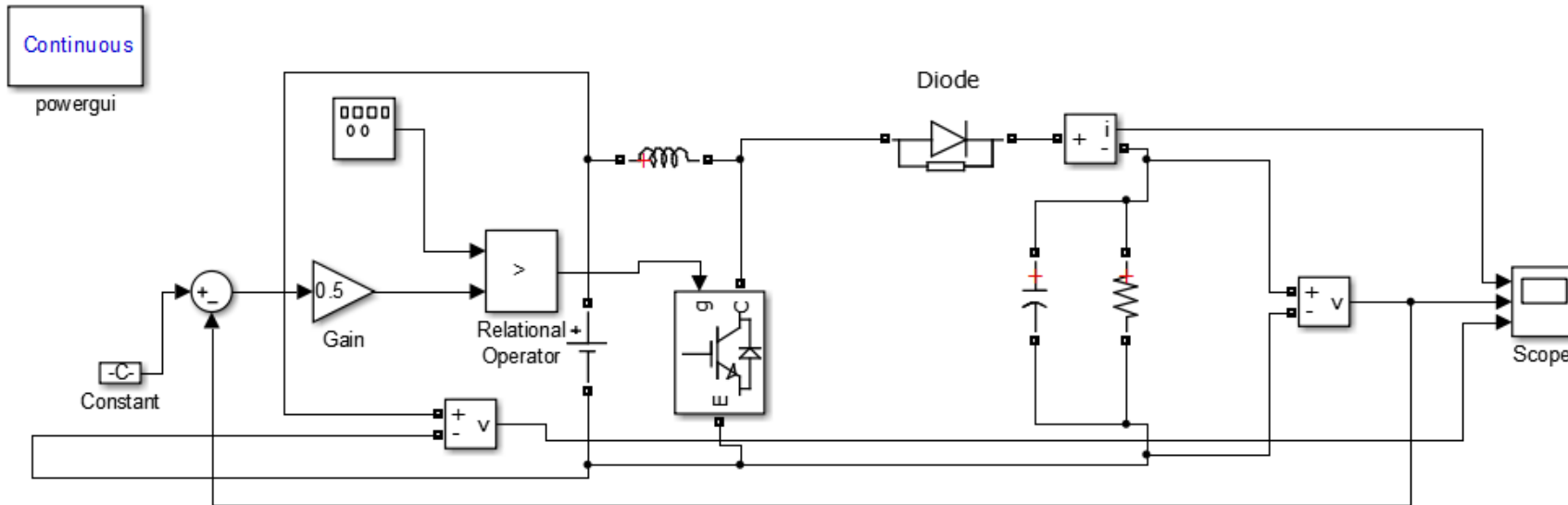



The parameters chosen are
 $V_{in}=220$, $V_{ref} = 330V$,
 $L=500 \mu H$, $C=100 \mu F$, $R=33-45 \Omega$,
 $\alpha=2$, $V_L=2V$, $V_U=5V$, $T=50 \mu s$;

Simulation Results:


Attractor at $V_i = 19.5$ V

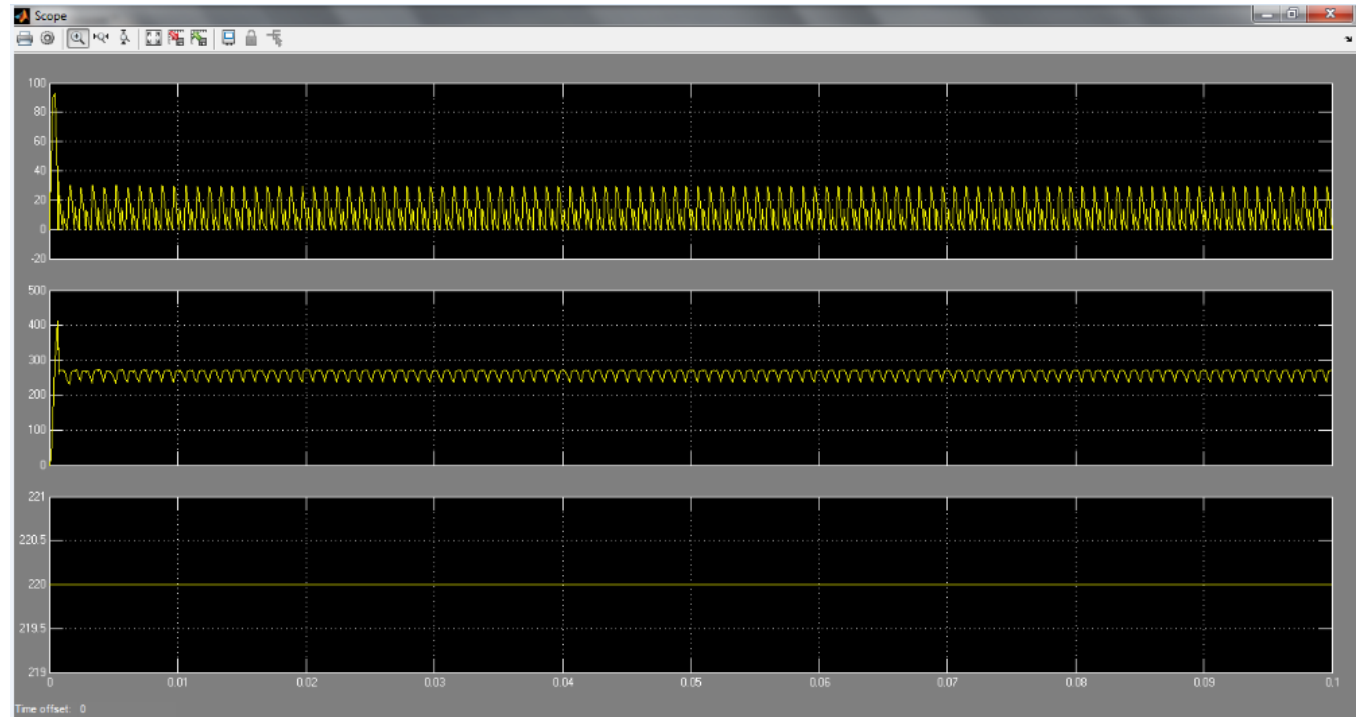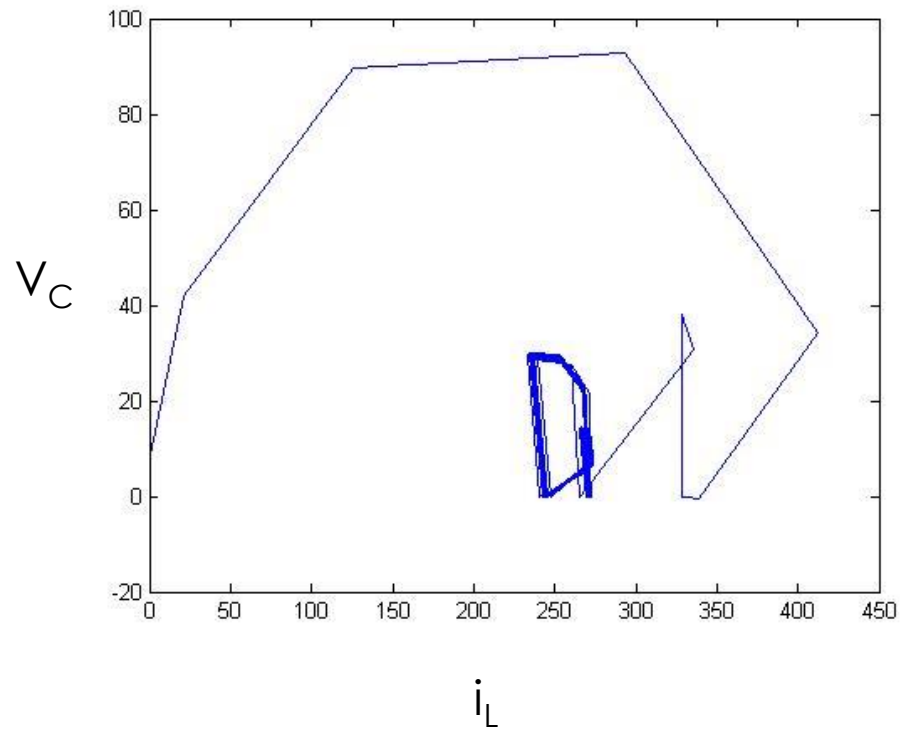

Simulation Results cont....

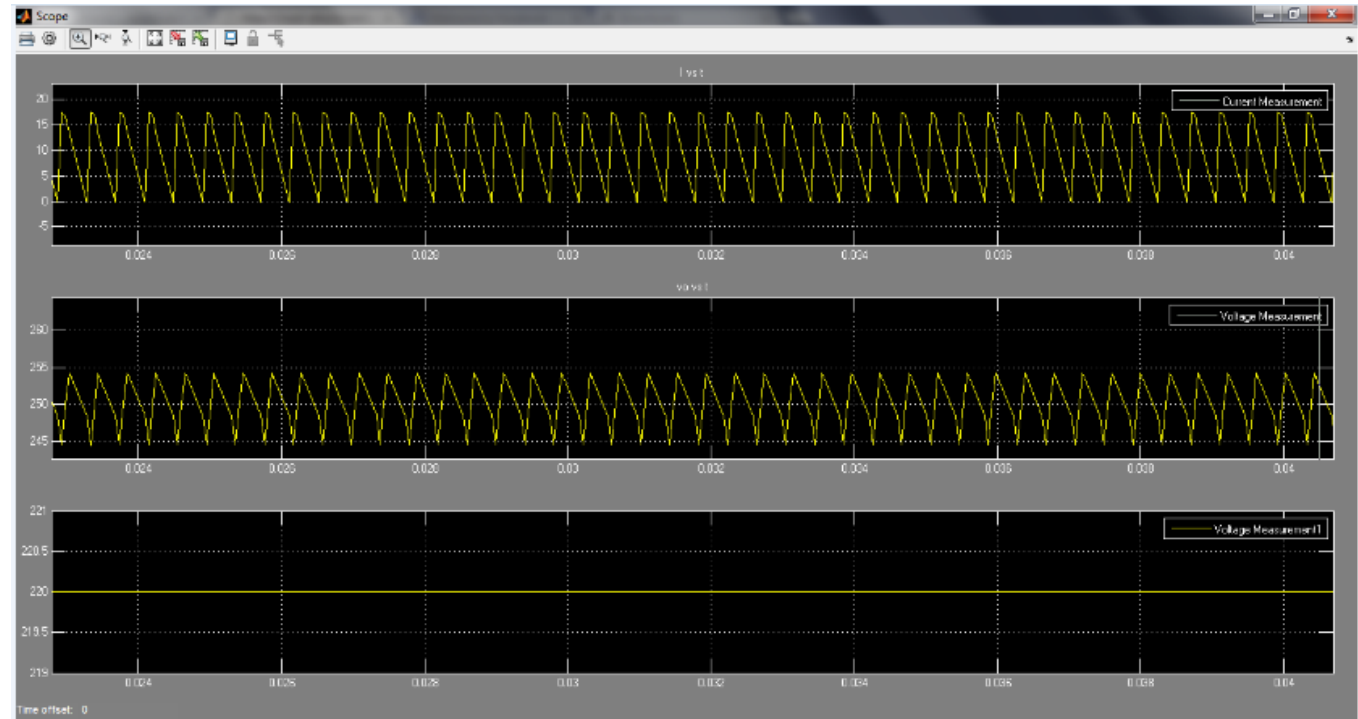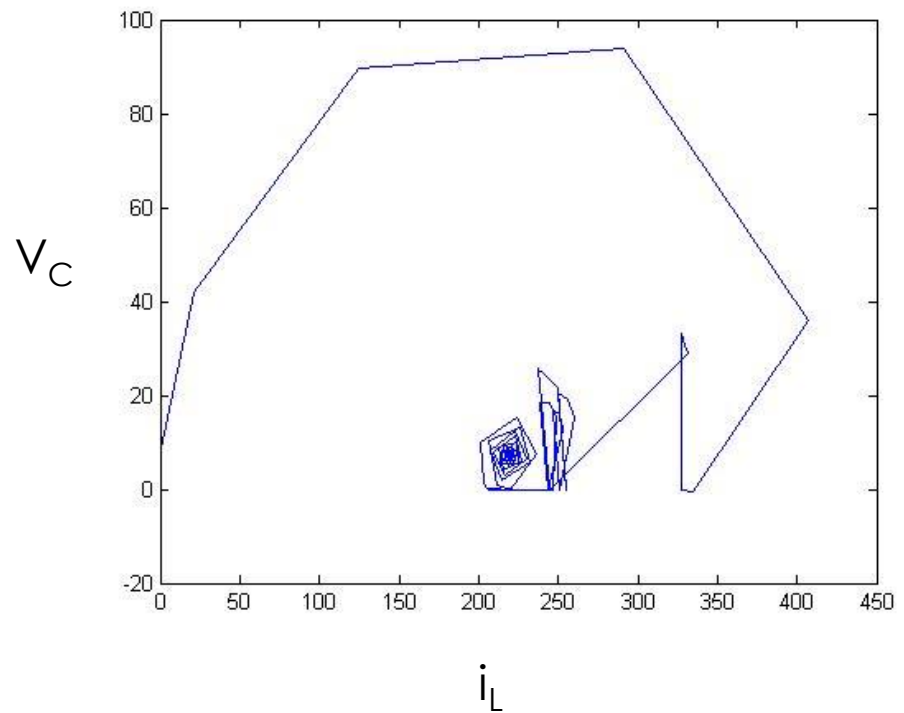


Bifurcation Diagram

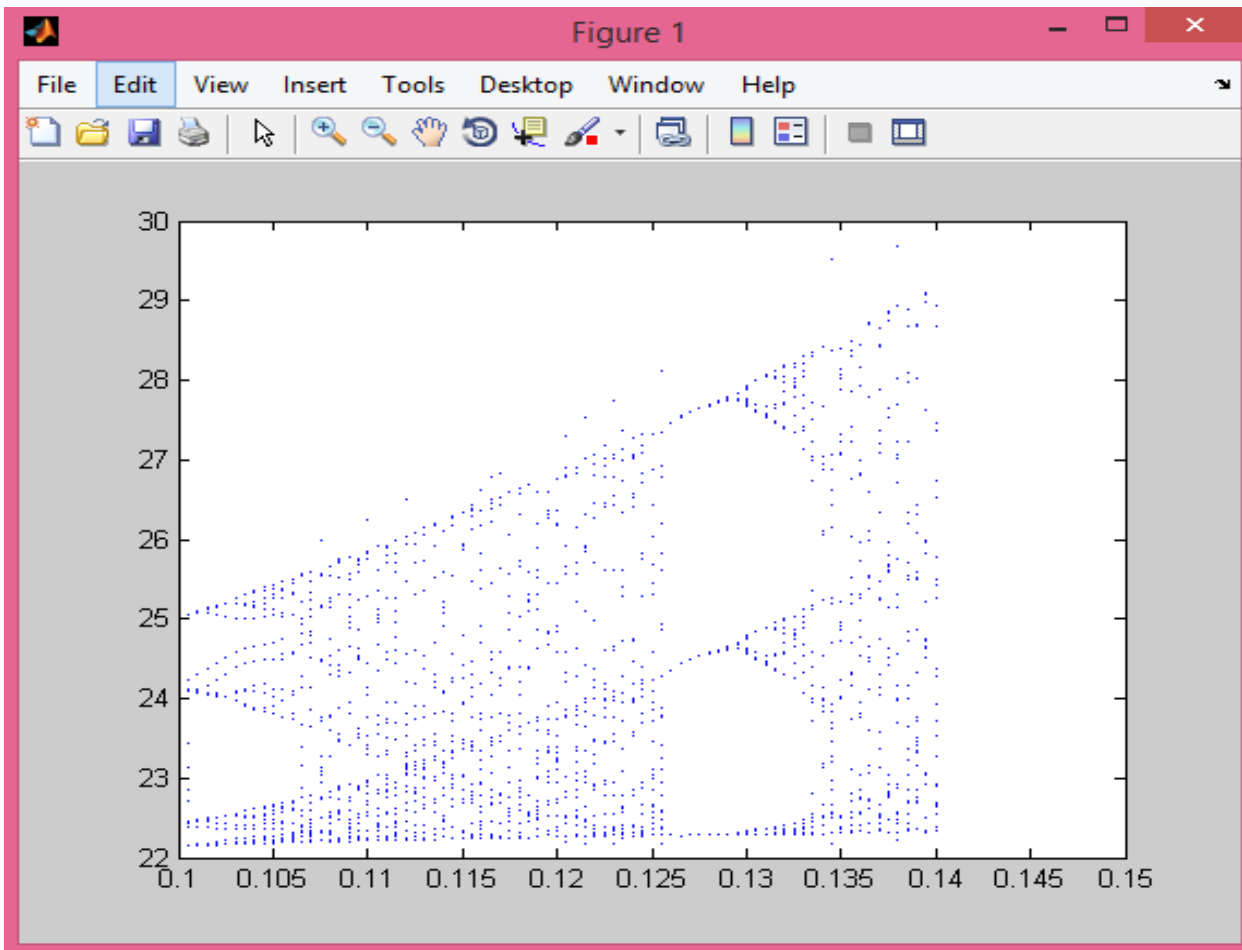

Gain 'a' was chosen as the bifurcation parameter. This diagram clearly shows that the period-doubling route to chaos as a reaches 0.14.

Buck-Boost Chopper

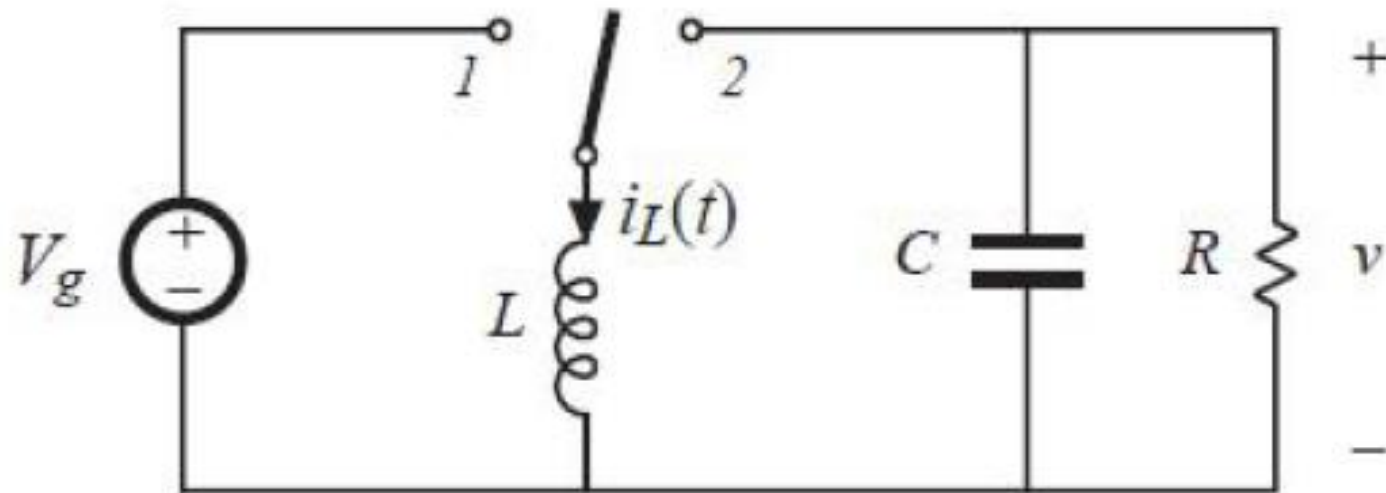

- ▶ The average value of $v_s(t)$, which would then be equal to DV_g . Therefore,

$$V_o = D/(1 - D)*V_g$$

Principle of Operation of a Buck-Boost Chopper


$$\begin{cases} \frac{di}{dt} = \frac{E}{L} \\ \frac{dv_c}{dt} = -\frac{1}{RC} v_c \end{cases}$$

When switch is closed

$$\begin{cases} \frac{di}{dt} = -\frac{1}{L} v_c \\ \frac{dv_c}{dt} = \frac{1}{C} i - \frac{1}{RC} v_c \end{cases}$$


When switch is open

Simulation of the Circuit – Closed Loop

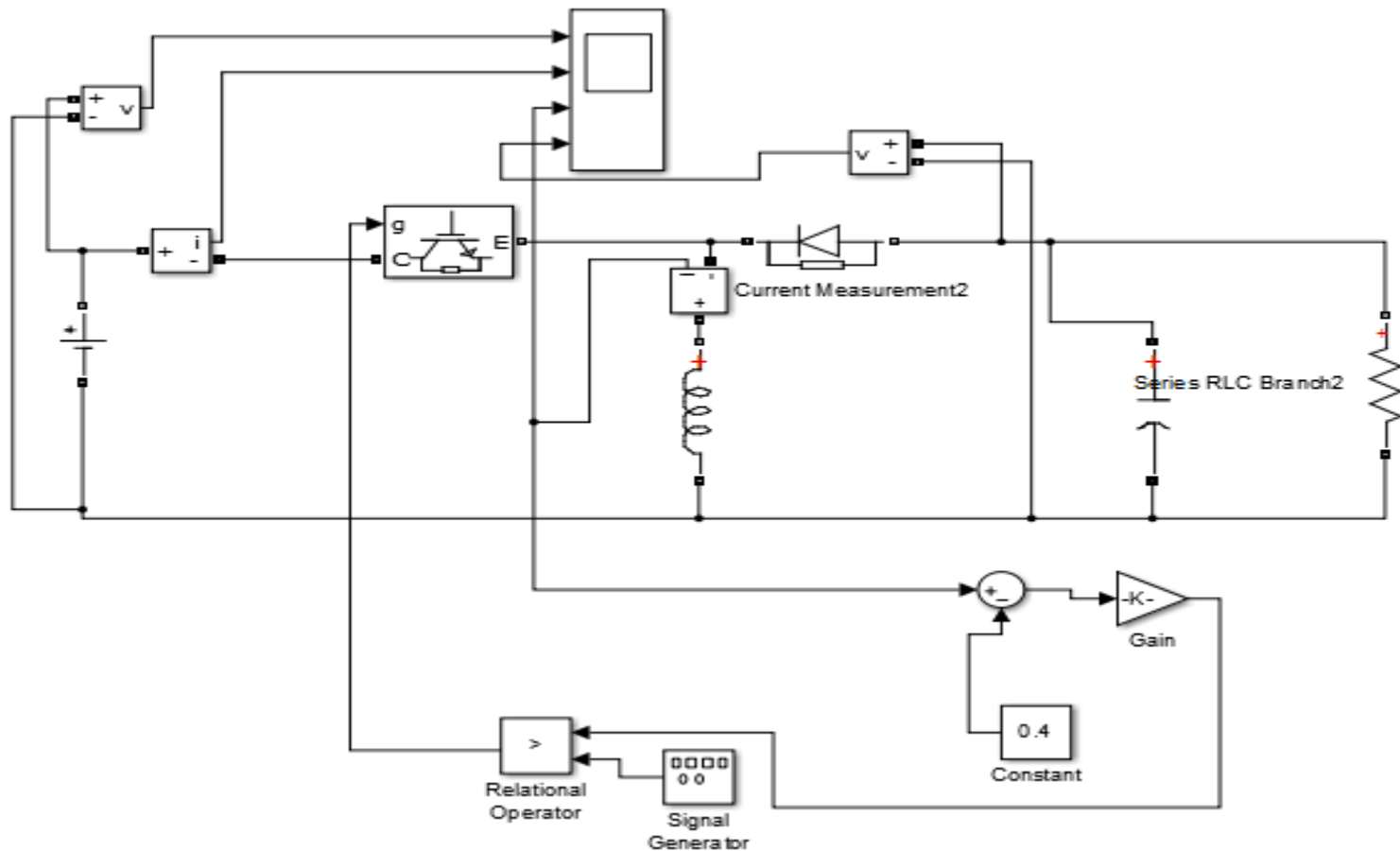


- ▶ The parameters chosen are $V_{in}=12\text{ V}$, $I_{ref}=4.5\text{ A}$, $L=1.1\text{ mH}$, $C=4.4\text{ }\mu\text{F}$, $R=50\text{ }\Omega$, $\alpha=2$, $V_L=2\text{ V}$, $V_U=5\text{ V}$, $T=50\text{ }\mu\text{s}$;

Chopper Open Loop

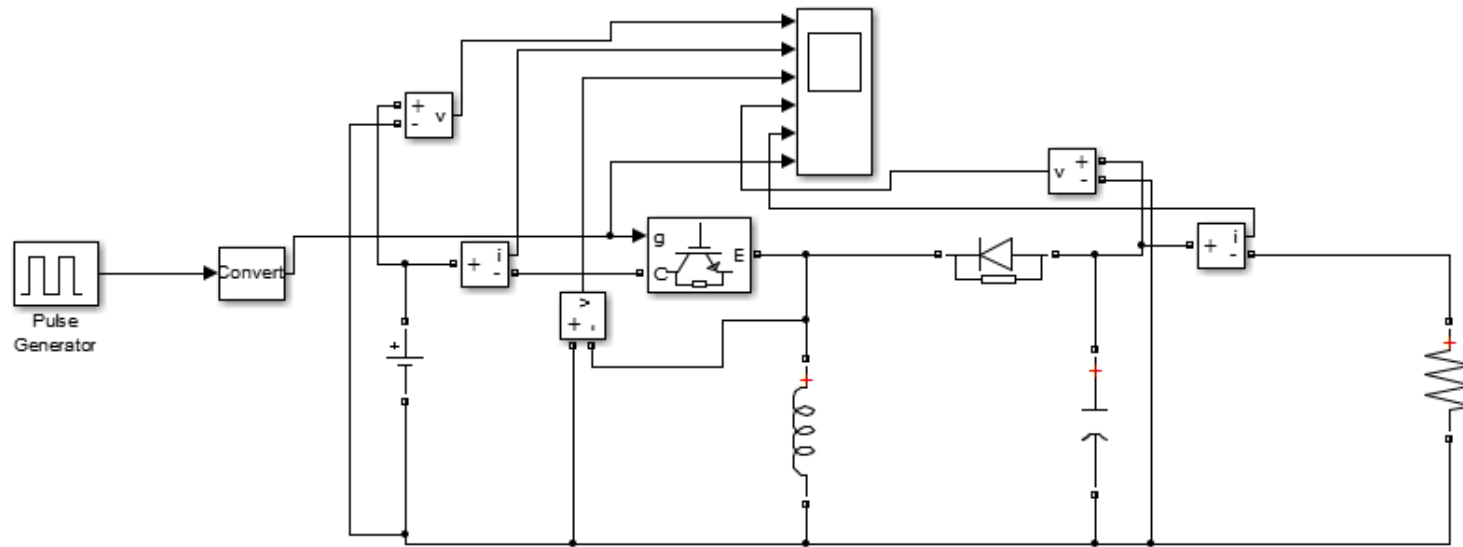


- The parameters chosen are $V_{in}=12\text{ V}$, $I_{ref}=4.5\text{ A}$, $L=1.1\text{ mH}$, $C=4.4\text{ }\mu\text{F}$, $R=50\text{ }\Omega$, $\alpha=2$, $V_L=2\text{ V}$, $V_U=5\text{ V}$, $T=50\text{ }\mu\text{s}$;

Simulation Results:

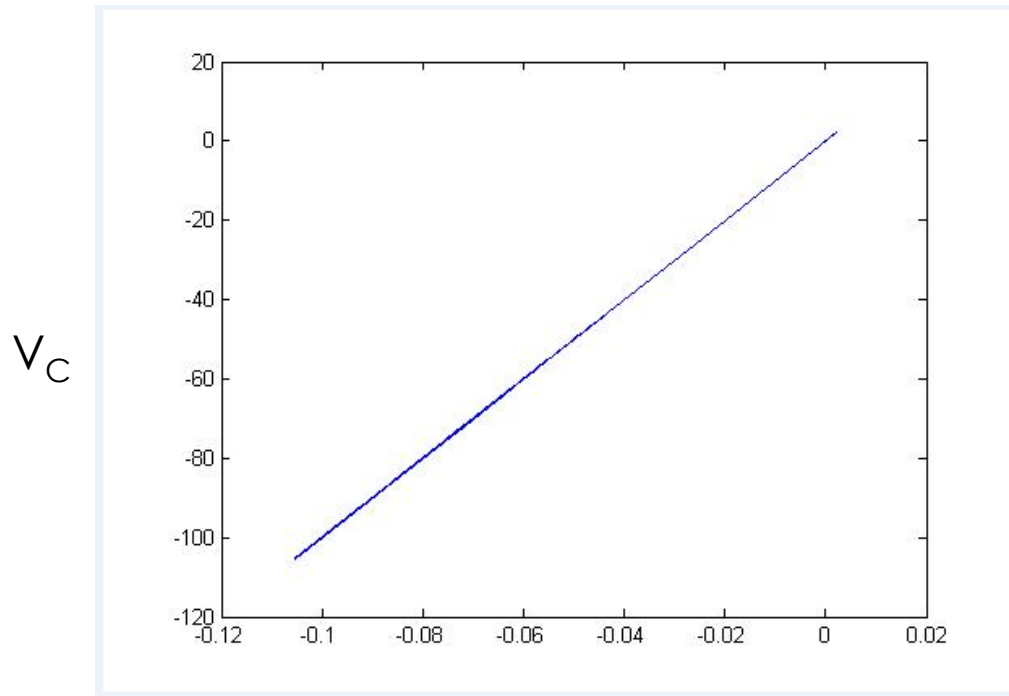


i_L
Open Loop

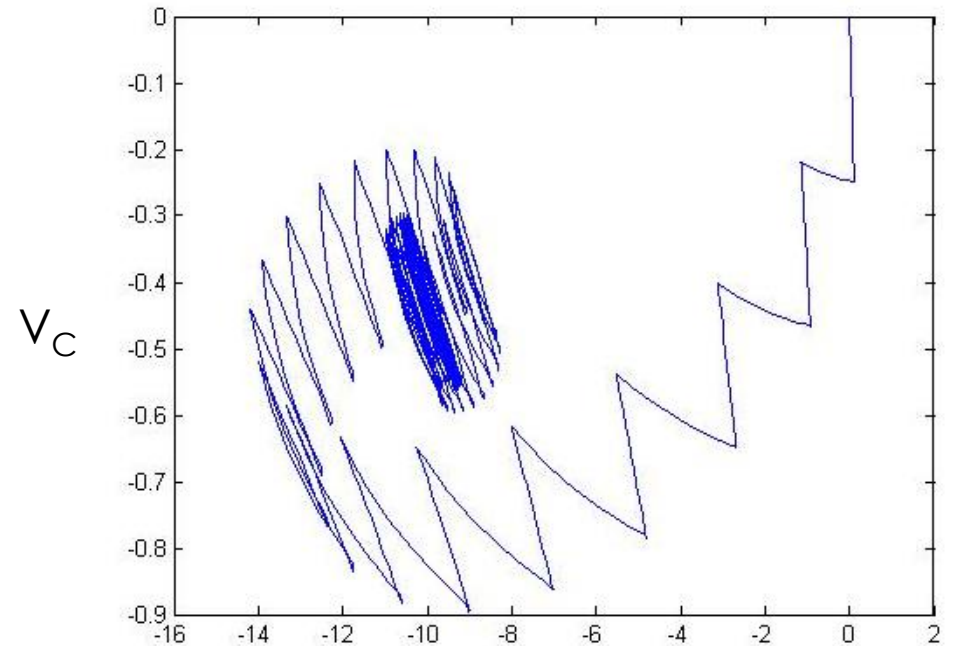


i_L
Closed Loop


Application 1: A laptop computer power supply system

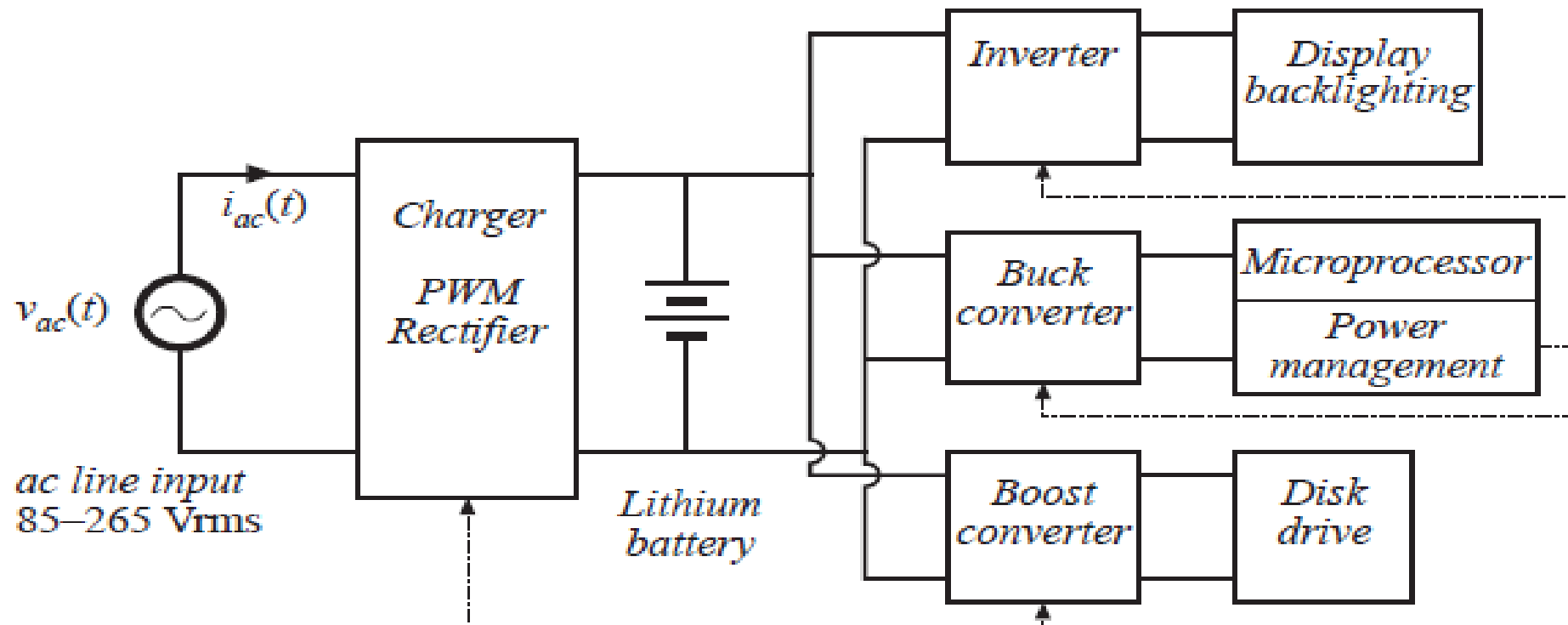

Application 2: Power system of an earth-orbiting spacecraft

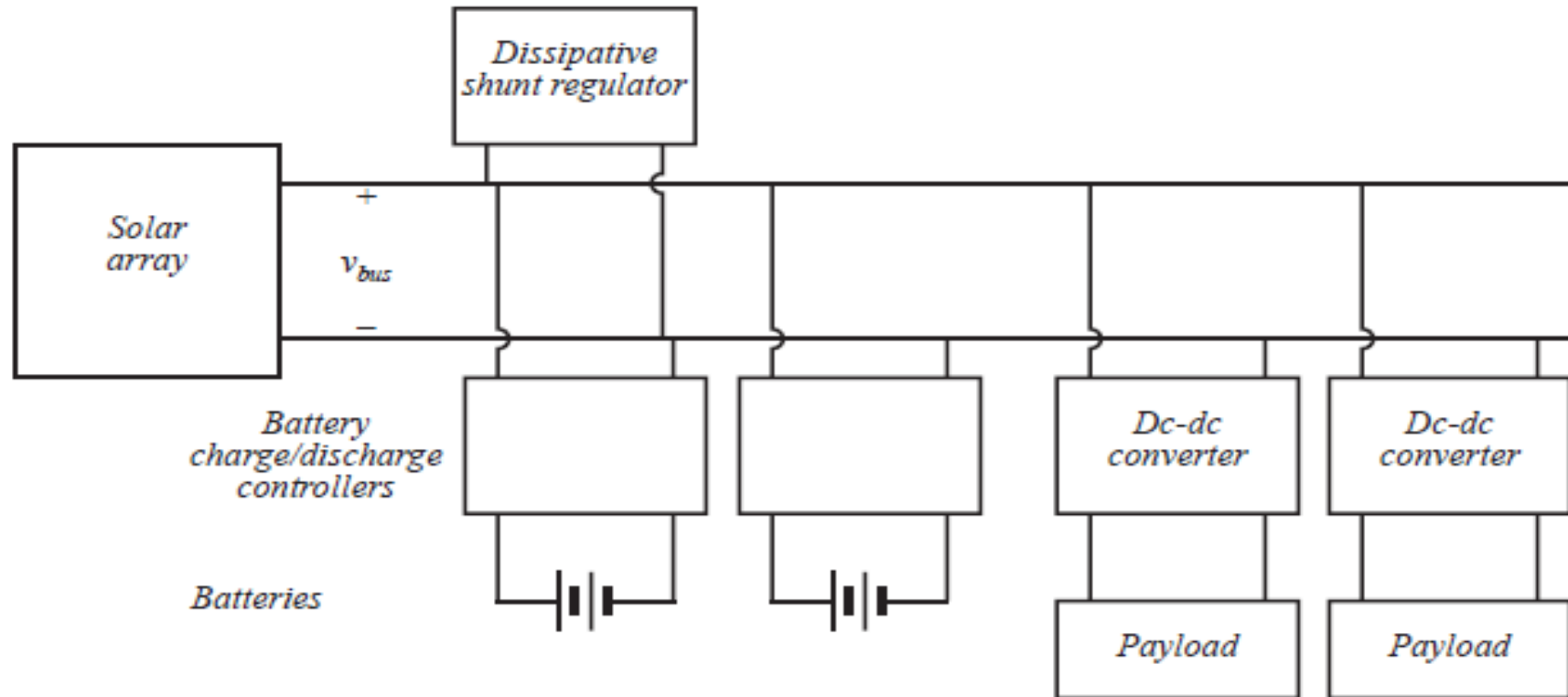

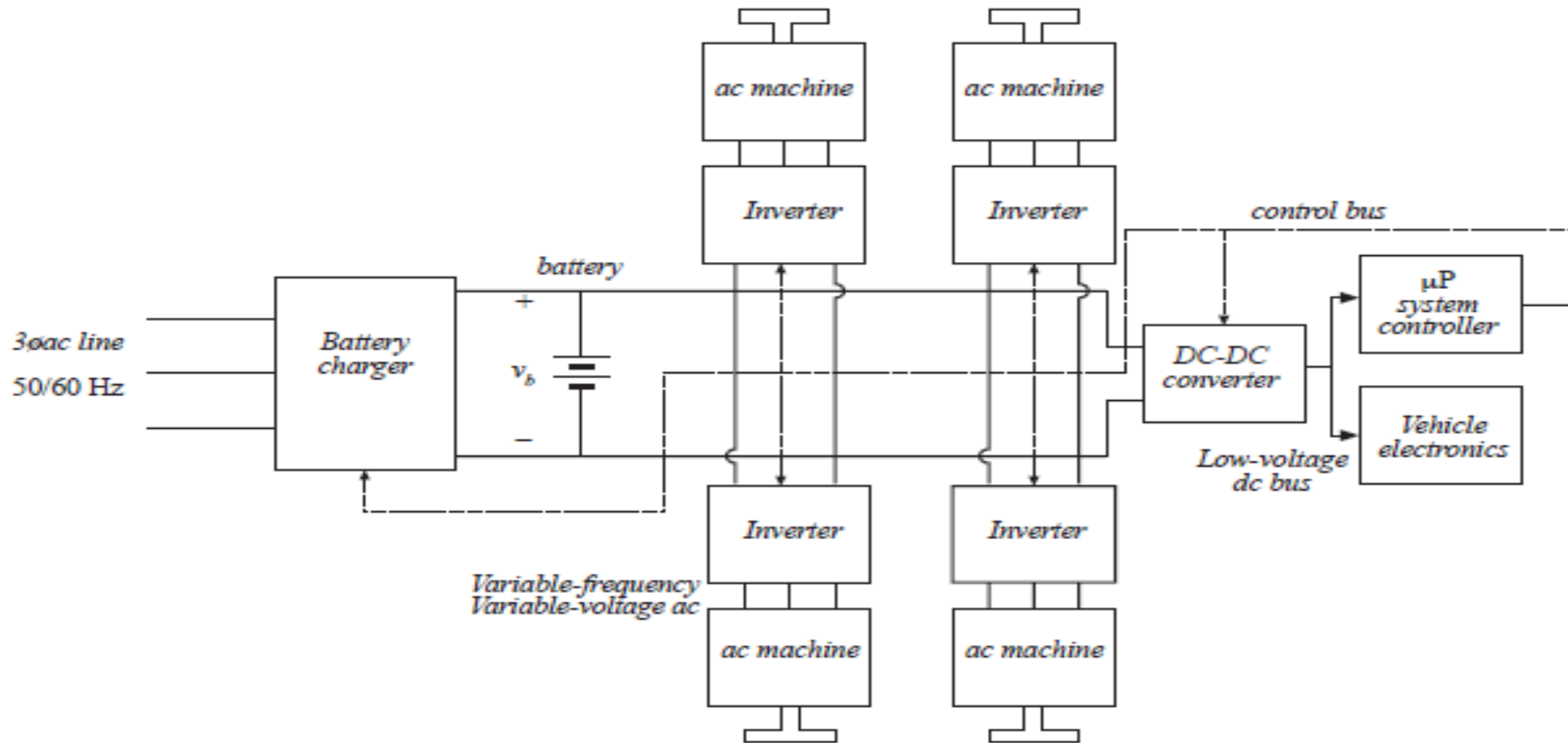Application 3: An electric vehicle power and drive system



References

- ▶ [1] di.Bernardo, M., Fosas, E., Olivar, G., Vasca, F. Secondary bifurcations and high-periodic orbits in voltage controlled buck converter // International Journal of Bifurcation and Chaos. - Vol.12, no.7 (1997) p.2755-2771.
- ▶ [2] Fosas, E., Olivar, G. Study of chaos in buck converter. IEEE Transactions on Circuits and Systems Part I. - Vol.43, no.1 (1996), p. 13-25.
- ▶ [3] Hammil, D.C., Deane, J.H.B., Jefferies, D.J. Modeling of chaotic dc/dc converters by iterative nonlinear mappings. IEEE Transactions on Circuits and Systems Part I. - Vol.35, no.8 (1992), p. 25-36.
- ▶ [4] C.K Tse, Complex Behaviour of Switching Power Converters. CRC Press, 2004.
- ▶ [5] M. di Bernardo, C.J. Budd, A.R. Champneys, and P. Kowalczyk. Piecewise-Smooth Dynamical Systems: Theory and Application, Springer –Verlag, Berlin, 2008.
- ▶ [6] M. Zakrzhevsky, "New concepts of nonlinear dynamics: complete bifurcation groups, protuberances, unstable periodic infinitiums and rare attractors," Journal of Vibroengineering, vol.10, iss.4 (2008), pp.421- 441.
- ▶ [7] Dmitry Pikulin, "The Complete Bifurcation Analysis of Boost DC-DC Converter", Scientific Journal of Riga Technical University Telecommunications and Electronics .



THANK YOU