

Indian Institute of Technology Jodhpur, Year 2018-2019

Digital Logic and Design

(Course Code: EE222)

Lecture 25-26: Sequential Circuits Contd..

**Course Instructor: Shree Prakash
Tiwari**

Email: sptiwari@iitj.ac.in

Webpage: <http://home.iitj.ac.in/~sptiwari/>

Course related documents will be uploaded on
<http://home.iitj.ac.in/~sptiwari/DLD/>

Note: The information provided in the slides are taken from text books Digital Electronics (including Mano & Ciletti), and various other resources from internet, for **teaching/academic use only**

1

State Assignment Problem

- Some state assignments are better than others.
- The state assignment influences the complexity of the state machine.
 - The combinational logic required in the state machine design is dependent on the state assignment.
- Types of state assignment
 - Binary encoding: 2^N states \rightarrow N Flip-Flops
 - Gray-code encoding: 2^N states \rightarrow N Flip-Flops
 - One-hot encoding: N states \rightarrow N Flip-Flops

FSM: State Assignment

Example:

Design a FSM that detects a sequence of two or more consecutive ones on an input bit stream.


The FSM should output a 1 when the sequence is detected, and a 0 otherwise.

This is another example of a *sequence detector*.

FSM: State Assignment

Input:	0 1 1 1 0 1 0 1 1 0 1 1 1 0 1 ...
Output:	0 0 1 1 0 0 0 0 1 0 0 1 1 0 0 ...

FSM: State Assignment

 

FSM: State Assignment

Present State	Next State		Output
	$w = 0$	$w = 1$	
S_0	S_0	S_1	0
S_1	S_0	S_2	0
S_2	S_0	S_2	1

State Table

FSM: State Assignment #1

State Assigned Table

Present State			Next State						Output
			w = 0			w = 1			
	Q_A	Q_B		Q_A^+	Q_B^+		Q_A^+	Q_B^+	z
S_0	0	0	S_0	0	0	S_1	0	1	0
S_1	0	1	S_0	0	0	S_2	1	0	0
S_2	1	0	S_0	0	0	S_2	1	0	1
	1	1		d	d		d	d	d

Using Binary Encoding
for the State Assignment

FSM: State Assignment #1

State Assigned Table

Present State			Next State				FF Inputs			
			w = 0		w = 1		w = 0		w = 1	
	Q_A	Q_B	Q_A^+	Q_B^+	Q_A^+	Q_B^+	D_A	D_B	D_A	D_B
S_0	0	0	0	0	0	1	0	0	0	1
S_1	0	1	0	0	1	0	0	0	1	0
S_2	1	0	0	0	1	0	0	0	1	0
	1	1	d	d	d	d	d	d	d	d

Characteristic Equation: $D = Q^+$

FSM: State Assignment #1

$$D_A$$

	$Q_A Q_B$	00	01	11	10
W	0	0	0	d	0
	1	0	1	d	1

$$D_A = W \cdot Q_B + W \cdot Q_A$$

$$D_A = W \cdot (Q_A + Q_B)$$

$$D_B$$

	$Q_A Q_B$	00	01	11	10
W	0	0	0	d	0
	1	1	0	d	0

$$D_B = W \cdot \bar{Q}_A \cdot \bar{Q}_B$$

FSM: State Assignment #1


$$Z$$

	Q_A	0	1
Q_B	0	0	1
	1	0	d

$$Z = Q_A$$

K-Map and Boolean expression for z

FSM: State Assignment #1

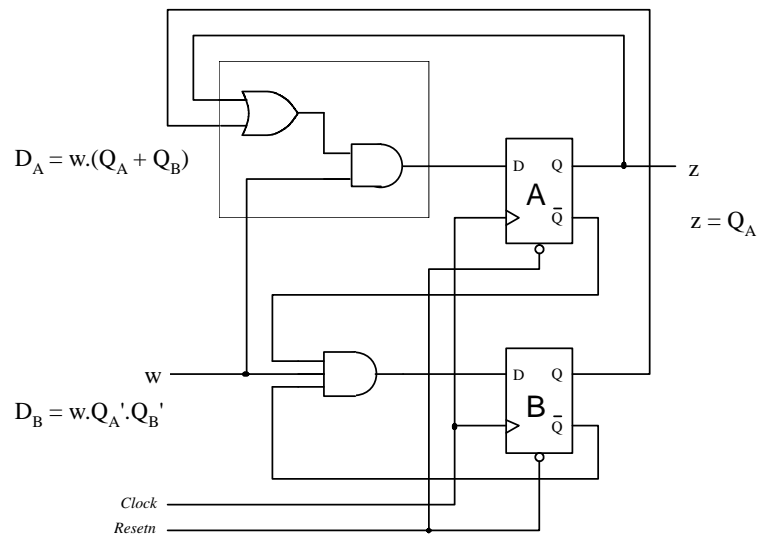

FSM: State Assignment #2

State Assigned Table

Present State			Next State						Output
			w = 0			w = 1			
	Q _A	Q _B		Q _A ⁺	Q _B ⁺		Q _A ⁺	Q _B ⁺	z
S ₀	0	0	S ₀	0	0	S ₁	0	1	0
S ₁	0	1	S ₀	0	0	S ₂	1	1	0
S ₂	1	1	S ₀	0	0	S ₂	1	1	1
	1	0		d	d		d	d	d

Using Gray-code Encoding for the State Assignment

FSM: State Assignment #2

State Assigned Table

Present State			Next State				FF Inputs			
			w = 0		w = 1		w = 0		w = 1	
	Q_A	Q_B	Q_A^+	Q_B^+	Q_A^+	Q_B^+	D_A	D_B	D_A	D_B
S_0	0	0	0	0	0	1	0	0	0	1
S_1	0	1	0	0	1	1	0	0	1	1
S_2	1	1	0	0	1	1	0	0	1	1
	1	0	d	d	d	d	d	d	d	d

Characteristic Equation: $D = Q^+$

FSM: State Assignment #2

D_A

	$Q_A Q_B$	00	01	11	10
w					
0		0	0	0	d
1		0	1	1	d

$$D_A = w \cdot Q_B$$

D_B

	$Q_A Q_B$	00	01	11	10
w					
0		0	0	0	d
1		1	1	1	d


$$D_B = w$$

z

	Q_A	0	1
Q_B			
0		0	d
1		0	1

$$z = Q_A$$

FSM: State Assignment #2

 

FSM: State Assignment #3

State Assigned Table

Present State				Next State							
				w = 0				w = 1			
	Q_A	Q_B	Q_C		Q_A^+	Q_B^+	Q_C^+		Q_A^+	Q_B^+	Q_C^+
S_0	0	0	1	S_0	0	0	1	S_1	0	1	0
S_1	0	1	0	S_0	0	0	1	S_2	1	0	0
S_2	1	0	0	S_0	0	0	1	S_2	1	0	0

Using One-hot Encoding
for the State Assignment


For each state only one flip-flop is set to 1.
The remaining combination of state variables are not used.

Characteristic Equation: $D = Q^+$

Finite State Machines: Other Examples

 - Example: Edge Detector


Bit are received one at a time (one per cycle),
such as: 000111010 $\xrightarrow{\text{time}}$



Design a circuit that asserts
its output for one cycle when
the input bit stream changes
from 0 to 1.

Try two different solutions.

State Transition Diagram Solution A

 

	IN	PS	NS	OUT
ZERO	0	00	00	0
	1	00	01	0
CHANGE	0	01	00	1
	1	01	11	1
ONE	0	11	00	0
	1	11	11	0

Solution A, circuit derivation


	IN	PS	NS	OUT
ZERO	0	00	00	0
	1	00	01	0
CHANGE	0	01	00	1
	1	01	11	1
ONE	0	11	00	0
	1	11	11	0

	PS	
	00 01 11 10	
IN	0	0 0 0 -
	1	0 1 1 -

$NS_1 = IN PS_0$

	PS	
	00 01 11 10	
IN	0	0 0 0 -
	1	1 1 1 -

$NS_0 = IN$

 


	PS	
	00 01 11 10	
IN	0	0 1 0 -
	1	0 1 0 -

$OUT = \overline{PS_1} PS_0$

Solution B

 
Output depends non only on PS but also on input, IN



Let ZERO=0,
ONE=1


IN	PS	NS	OUT
0	0	0	0
0	1	0	0
1	0	1	1
1	1	1	0

$$NS = IN, OUT = IN PS'$$

 

What's the *intuition* about this solution?

Edge detector timing diagrams

 


- **Solution A: output follows the clock**
- **Solution B: output changes with input rising edge and is asynchronous wrt the clock.**

FSM Comparison

Solution A

Moore Machine

 
- **output function only of PS**
- **maybe more state**
- **synchronous outputs**
 - no glitching
 - one cycle "delay"
 - full cycle of stable output




Solution B

Mealy Machine

 - **output function of both PS & input**
- **maybe fewer states**
- **asynchronous outputs**
 - if input glitches, so does output
 - output immediately available
 - output may not be stable long enough to be useful:



FSM Recap

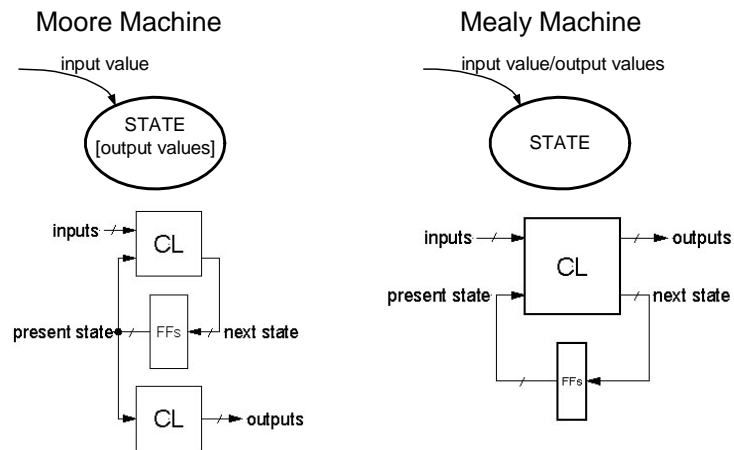

Both machine types allow one-hot implementations.

What next.....

- **Sequential Circuits contd...**

Overview

- Important to minimize the size of digital circuitry
- Analysis of state machines leads to a state table (or diagram)
- In many cases reducing the number of states reduces the number of gates and flops
 - This is not true 100% of the time
- We attempt **state reduction** by examining the state table
- Other, more advanced approaches, possible
- Reducing the number of states generally reduces complexity.

FSM Optimization

◦ State Reduction:


Motivation:

lower cost

- fewer flip-flops in one-hot implementations
- possibly fewer flip-flops in encoded implementations
- more don't cares in next state logic
- fewer gates in next state logic

Simpler to design with extra states then reduce later.

◦ Example: Odd parity checker

 

State Reduction


- “Row Matching” is based on the state-transition table:
- If two states
 - have the same output *and* both transition to the same next state
 - or both transition to each other
 - or both self-loop
 - then they are equivalent.
- Combine the equivalent states into a new renamed state.
- Repeat until no more states are combined

PS	NS		output
	x=0	x=1	
S0	S0	S1	0
S1	S1	S2	1
S2	S2	S1	0


FSM Optimization

- Merge state S2 into S0
- Example: Odd parity checker.
- Eliminate S2
- New state machine shows same I/O behavior

PS	NS		output
	x=0	x=1	
S0	S0	S1	0
S1	S1	S0	1

 

Row Matching Example

 

State Transition Table


PS	NS		output	
	x=0	x=1	x=0	x=1
a	a	b	0	0
b	c	d	0	0
c	a	d	0	0
d	e	f	0	1
e	a	f	0	1
f	g	f	0	1
g	a	f	0	1

Row Matching Example

PS	NS		output	
	x=0	x=1	x=0	x=1
a	a	b	0	0
b	c	d	0	0
c	a	d	0	0
d	e	f	0	1
e	a	f	0	1
f	e	f	0	1

PS	NS		output	
	x=0	x=1	x=0	x=1
a	a	b	0	0
b	c	d	0	0
c	a	d	0	0
d	e	d	0	1
e	a	d	0	1

Reduced State Transition Diagram

 

State Reduction

- The “row matching” method is not guaranteed to result in the optimal solution in all cases, because it only looks at pairs of states.
- Another method guarantees the optimal solution:
- “Implication table” method:
 Read Mano, chapter 9.
 Submit one page as assignment

Encoding State Variables

- Option 1: Binary values
 - 000, 001, 010, 011, 100 ...
- Option 2: Gray code
 - 000, 001, 011, 010, 110 ...
- Option 3: One hot encoding
 - One bit for every state
 - Only one bit is a one at a given time
 - For a 5-state machine
 - 00001, 00010, 00100, 01000, 10000

Summary

- Important to create smallest possible FSMs
- This course: use visual inspection method
- Often possible to reduce logic and flip flops
- State encoding is important